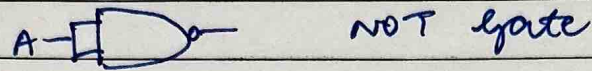


Assignment 1Mission 1)

a) $\text{NAND}(A, A) = \text{NOT}(A)$



b) $\text{NOT}(\text{NAND}(A, B)) = A \text{ AND } B$

c) $A + B = \overline{A \cdot B}$

$\text{NAND}(\text{NAND}(A, A), \text{NAND}(B, B)) = A \text{ OR } B$

Mission 2) Truth table

A	B	Sum(S)	Carry(C)
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Boolean expression -

$C = A \cdot B$

$S = A \oplus B$

Circuit = XOR + AND

Mission 3)


Truth Table

S_1	S_0	Output
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

MUX_0 Input = I_0, I_1
Select = S_0
Output = Y_0


MUX_1 Input = I_2, I_3
Select = S_0
Output = Y_1

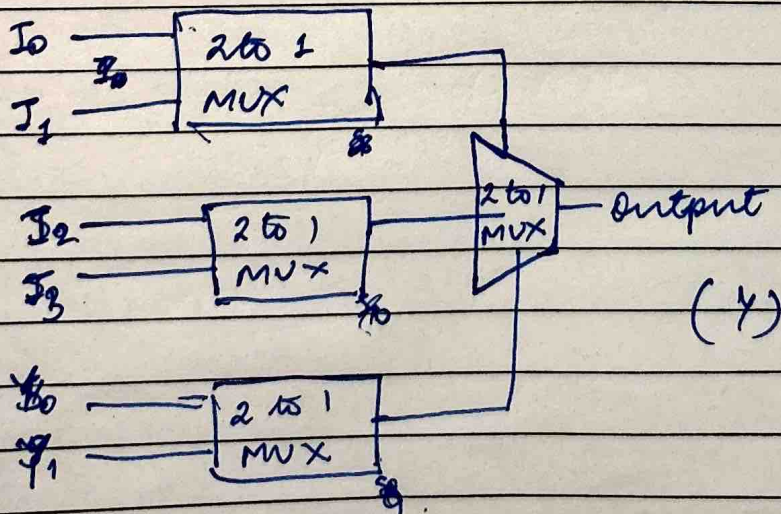MUX_2 Input = Y_0, Y_1
Select = S_1
Output = Y



Mission 4 a) current input $x(t)$
prev. $x(t-1)$ and $x(t-2)$

circuit can keep $x(t-1)$ and $x(t-2)$
 \Rightarrow 2 D flip flops to decide last 3
 inputs (1 1 1)

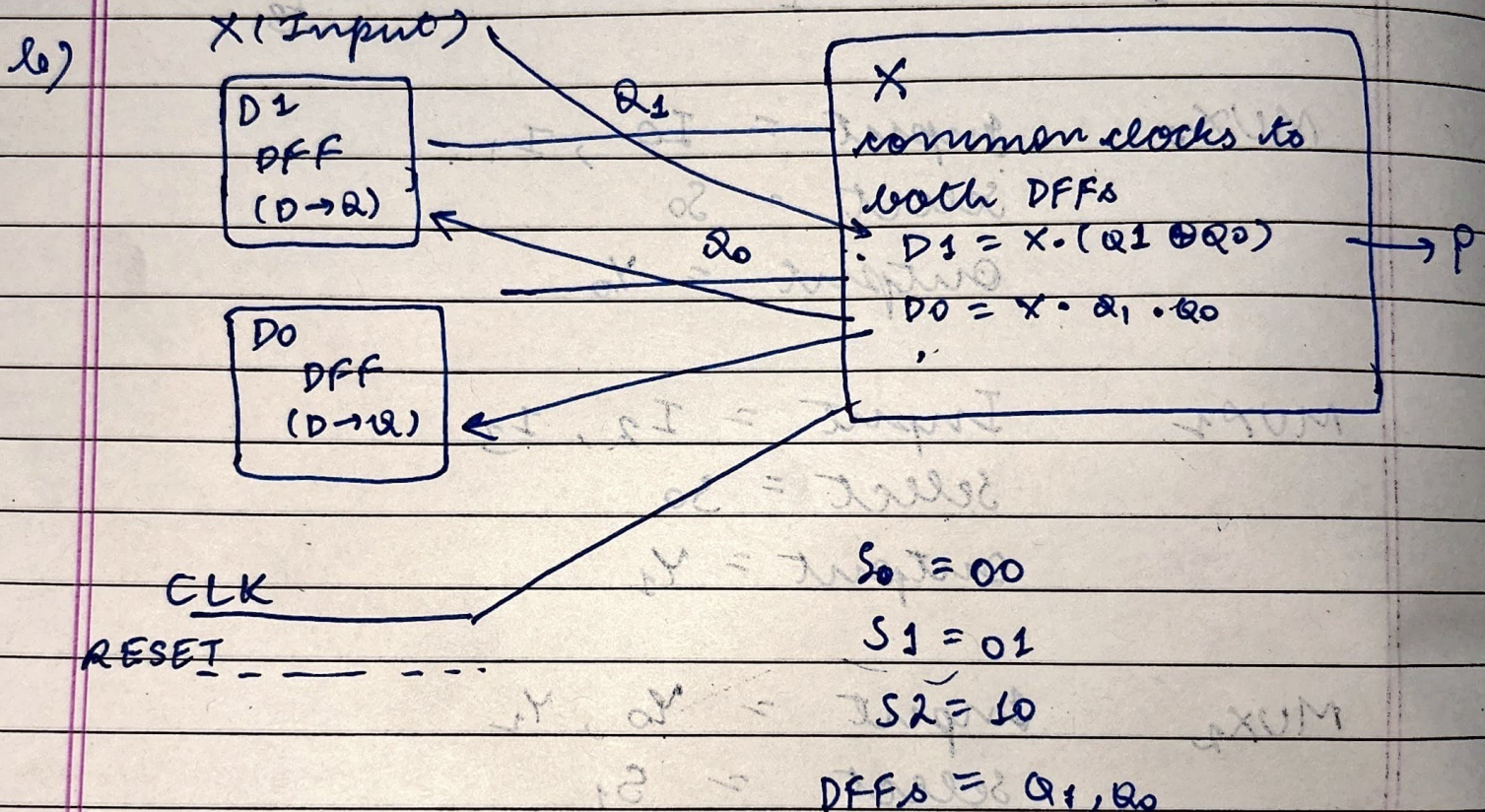

Mission 5

Q_1 toggles when $Q_0 = 1$

a) Current $Q_1 Q_0$

00

01

10

11

Next $Q_1 Q_0$

01

10

11

00

b)

$$D_0 = \bar{Q}_0$$

$$D_1 = Q_1 \oplus Q_0$$

c)

